

Solution TD N° 03

Exo 1. Triangle de puissance

$$v(t) = 150 \sin(\omega t + 10^\circ) \rightarrow \bar{V} = \left(\frac{150}{\sqrt{2}} \right) \angle 10^\circ \text{ V}$$

$$i(t) = 5 \sin(\omega t - 50^\circ) \rightarrow \bar{I} = \left(\frac{5}{\sqrt{2}} \right) \angle -50^\circ \text{ A}$$

La puissance complexe est:

$$\bar{S} = \bar{V} \cdot \bar{I}^* = \left(\frac{150}{\sqrt{2}} \cdot \frac{5}{\sqrt{2}} \right) \angle 10^\circ + 50^\circ = 375 \angle 60^\circ \text{ VA}$$

$$\bar{S} = P + jQ = 187,5 + j325 \text{ VA}$$

$$P = \text{Re}(\bar{S}) = 187,5 \text{ W}$$

$$Q = \text{Im}(\bar{S}) = 325 \text{ vars inductifs}$$

$$S = |\bar{S}| = 375 \text{ VA}$$

$$\text{F.P.} = \cos 60^\circ = 0,5 \text{ inductif}$$

Exo 2

$$v(t) = 99 \sin(6000t + 30^\circ) \rightarrow \bar{V} = \left(\frac{99}{\sqrt{2}} \right) \angle 30^\circ = 70 \angle 30^\circ \text{ V}$$

La puissance active est:

$$P = V I \cos \phi \Rightarrow I = \frac{P}{V \cos \phi} = \frac{940}{70 \cdot 0,707} = 19 \text{ A}$$

Le courant est en avance de $\arccos(0,707) = 45^\circ$ sur la tension $\Rightarrow \bar{I} = 19 \angle 75^\circ \text{ A}$

L'impédance du circuit est: $\bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{70 \angle 30^\circ}{19 \angle 75^\circ} = 3,68 \angle -45^\circ$

$$\bar{Z} = 2,6 - j2,6 \Omega$$

Comme $\bar{Z} = R - jX_C$ / $X_C = \frac{1}{\omega C}$


$$R = 2,6 \Omega \text{ et } C = \frac{1}{\omega X_C} = \frac{1}{6000 \cdot 2,6} = 64,1 \mu\text{F}$$

Exo 3

$$\bar{Z} = 3 + 6j - 2j = 3 + 4j$$

$$\bar{Z} = 5 \angle 53,1^\circ \Omega$$
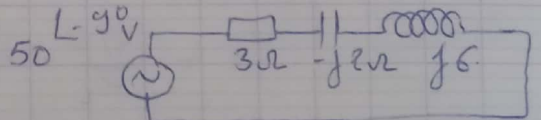
$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{50 \angle -90^\circ}{5 \angle 53,1^\circ} = 10 \angle -143,1^\circ \text{ A}$$



La puissance apparente $\bar{S} = \bar{V} \cdot \bar{I}^* = 50 \angle -90^\circ \cdot 10 \angle 143,1^\circ = 500 \angle 53,1^\circ \text{ VA}$

$$\bar{S} = 300 + j400 \text{ VA}$$

$$\vec{S} = P + jQ \Rightarrow P = 300 \text{ W}, Q = 400 \text{ Vars}$$

$P = 300 \text{ W}$

$$\cos \epsilon = 0.6 \rightarrow \epsilon = 53.1 \text{ degrees}$$

ou méthode

$$P = R I^2 = 3 \cdot 10^2 = 300 \text{ W}$$

$$Q = Q_{Cj} + Q_{-2j} = 6 \cdot 10^2 - 2 \cdot 10^2 = 400 \text{ Vars}$$

Ex 4

$$I = 30 \text{ A}$$

On suppose que la phase du courant I est choisie comme grandeur de référence $\Rightarrow I = 30 \text{ A}^{\angle 0^\circ}$

On a un diviseur de courant

$$\vec{I}_1 = 30 \angle 0^\circ \cdot \left(\frac{5 - 3j}{9 - 3j} \right) = 18,45 \text{ A} \angle 12,55^\circ$$

$$\vec{I}_2 = 30 \angle 0^\circ \cdot \left(\frac{4}{9 - 3j} \right) = 12,7 \text{ A} \angle 19,45^\circ$$

$$P = P_4 + P_5 = R_4 I_2^2 + R_5 I_1^2 = 4 (12,7)^2 + 5 (18,45)^2 = 2165 \text{ W}$$

$$Q = X I_1^2 = 3 (12,7)^2 = 483 \text{ Vars capacitifs}$$

$$\vec{S} = P - jQ = 2165 - j483 = 2210 \angle -12,16^\circ \Rightarrow S = 2210 \text{ VA}$$


$$F.P = \cos \phi = \frac{P}{S} = \frac{2165}{2210} = 0,98 \text{ capacitifs}$$

Ex 5

$$P = 1100 \text{ W}$$

$$\vec{I}_1 = \frac{\vec{V}}{Z_1} = \frac{\vec{V}}{3 + 4j} = \frac{\vec{V}}{5 \angle 53,1^\circ}$$
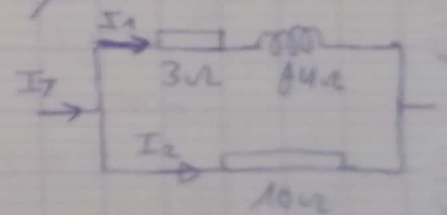
$$\vec{I}_2 = \frac{\vec{V}}{Z_2} = \frac{\vec{V}}{10}$$



Le rapport des modules des courants est $\frac{I_1}{I_2} = \frac{V/5}{V/10} = \frac{2}{1}$

$$\frac{P_3}{P_0} = \frac{R_3 I_1^2}{R_{10} I_2^2} = \frac{3}{10} \left(\frac{2}{1} \right)^2 = \frac{6}{5}$$

$$P_T = P_3 + P_{10} \Rightarrow \frac{P_T}{P_{10}} = \frac{P_3}{P_{10}} + 1$$

On remplace $\frac{P_3}{P_{10}}$ par $\frac{6}{5}$ $\frac{1100}{P_{10}} = \frac{6}{5} + 1$

$$\Rightarrow P_{10} = 1100 \left(\frac{5}{11} \right) = 500 \text{ W}$$

$$P_3 = 1100 - 500 = 600 \text{ W}$$

Suite exo 5.

$$P_3 = R I_1^2 \Rightarrow I_1 = \sqrt{\frac{P_3}{3}} = \sqrt{\frac{600}{3}} = 14,14 \text{ A}$$

si on pose $\bar{V} = \sqrt{L^0}$

$$\bar{I}_1 = 14,14 \angle -53,1 = 8,48 - j 11,31 \text{ A}$$


$$\bar{I}_2 = \frac{\bar{I}_1}{2} =$$

$$I_2 = \frac{I_1}{2} = 7,07 \Rightarrow \bar{I}_2 = 7,07 \angle 0^\circ \text{ A}$$

$$\bar{I}_T = \bar{I}_1 + \bar{I}_2 = 15,55 - j 11,31 = 19,25 \angle -36^\circ \text{ A}$$

Exo 6: Triangle de puissance pour chacune des branches pour la branche 1.
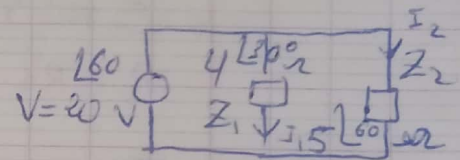
$$\bar{I}_1 = \frac{\bar{V}}{Z_1} = \frac{20 \angle 60}{4 \angle 30} = 5 \angle 30^\circ \text{ A}$$



$$\bar{S}_1 = \bar{V}_1 \bar{I}_1^* = 20 \angle 60 \times 5 \angle -30 = 100 \angle 30 = 86,6 + j 50 \text{ VA}$$

$P_1 = 86,6 \text{ W}$ $\Phi = 50 \text{ Var inductif}$ $S_1 = 100 \text{ VA}$

$FP_1 = 0,86 \text{ inductif}$


pour la branche 2.

$$\bar{I}_2 = \frac{\bar{V}}{Z_2} = \frac{20 \angle 60}{5 \angle 60} = 4 \angle 0^\circ \text{ A}$$

$$S_2 = \bar{V}_2 \bar{I}_2^* = 20 \angle 60 \cdot 4 \angle 0 = 80 \angle 60 = 40 + j 69,2 \text{ VA}$$

$P_2 = 40 \text{ W}$ $\Phi_2 = 69,2 \text{ Var}$ $S_2 = 80 \text{ VA}$ $FP_2 = \cos 60 = 0,5 \text{ ind}$

$P_1 = 86,6 \text{ W}$

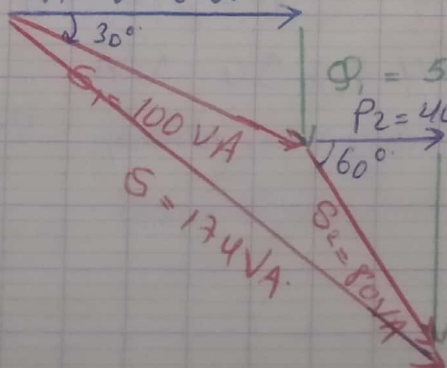

$\Phi_1 = 50 \text{ Var ind}$

$P_T = P_1 + P_2 = 86,6 + 40 = 126,6 \text{ W}$


$\Phi_T = \Phi_1 + \Phi_2 = 50 + 69,2 = 119,2 \text{ Var inductif}$

$\Phi_2 = 69,2 \text{ Var ind}$

$\bar{S}_T = \bar{P}_T + j \bar{\Phi}_T = 126,6 + j 119,2$

$S_T = 174 \text{ VA}$

Ex 7: $\eta = 85\%$ $P_{\text{sortie}} = 1492 \text{ W}$ F.P. = 0,8 inductif.

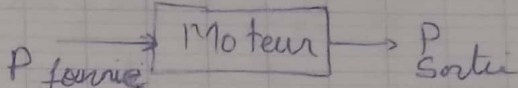$\eta = \frac{P_{\text{sortie}}}{P_{\text{fournie}}} \Rightarrow$ 

$P_{\text{fournie}} = \frac{P_{\text{sortie}}}{\eta} = \frac{1492}{0,85} = 1755 \text{ W}$


$P = S \cos \epsilon \Rightarrow S = \frac{P}{\cos \epsilon} = \frac{1755}{0,8} = 2190 \text{ V.A}$

$\epsilon = \arccos(0,8) = 36,9^\circ$

$\phi = S \sin \epsilon = 2190 \cdot \sin(36,9^\circ) = 1315 \text{ var inductifs}$

Ex no 8: $P_2 = 20 \text{ W}$

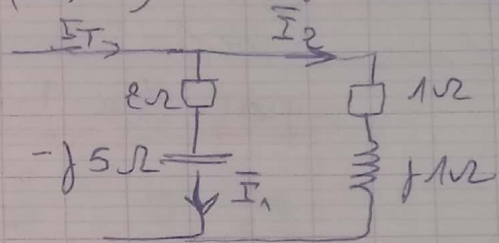$P_2 = R_2 \cdot I_1^2 \Rightarrow I_1 = \sqrt{\frac{P_2}{R_2}} = 3,16 \text{ A}$



$\bar{Z}_1 = 2 - 5j = 5,38 \angle -68,2^\circ$

On prend $\bar{V} = V \angle 0^\circ$

$\bar{V} = \bar{Z}_1 \cdot \bar{I}_1 \Rightarrow V = Z_1 \cdot I_1 = 5,38 \cdot 3,16 = 17 \text{ V}$

$\bar{V} = 17 \angle 0^\circ$, $\bar{I}_1 = 3,16 \angle +68,12^\circ = 1,173 + j2,934 \text{ A}$

$I_2 = \frac{\bar{V}}{Z_2} = \frac{17 \angle 0^\circ}{\sqrt{2} \angle 45^\circ} = 12 \angle -45^\circ \text{ A} = 8,485 - j8,485 \text{ A}$

$I_T = \bar{I}_1 + \bar{I}_2 = 11,1 \angle -29,8^\circ \text{ A}$

$\bar{S}_T = \bar{V}_0 \cdot \bar{I}_T^* = 17 \angle 0^\circ \cdot 11,1 \angle 29,8^\circ = 189 \angle 29,8^\circ$
 $= 164 + j94 \text{ VA}$

$P_T = 164 \text{ W}$, $\phi_T = 94 \text{ var inductifs}$, $S_T = 189 \text{ VA}$
 $F_p = 0,86 \text{ inductifs}$

ϵ no 09.

charge 1: $S_1 = 250 \text{ VA}$ $FP = 0,5$ inductif

$P_1 = S_1 \cos \epsilon_1 = 250 \cdot 0,5 = 125 \text{ W}$

$\epsilon_1 = \arccos 0,5 = 60^\circ \Rightarrow \sin \epsilon_1 = 0,86$

$Q_1 = S_1 \sin \epsilon_1 = 250 \times 0,86 = 216 \text{ vars inductifs}$

charge 2: $P_2 = 180 \text{ W}$, $FP = 0,8$ capacitive

$S_2 = \frac{P_2}{\cos \epsilon_2} = \frac{180}{0,8} = 225 \text{ VA}$

$\epsilon_2 = \arccos 0,8 = 36,9^\circ$

$Q_2 = 225 \sin 36,9 = 135 \text{ vars capacitifs}$

charge 3: $S_3 = 300 \text{ VA}$, $Q_3 = 100 \text{ vars inductifs}$

$\epsilon_3 = \arcsin \left(\frac{Q_3}{S_3} \right) = \arcsin \left(\frac{100}{300} \right) = 19,5^\circ$

$P_3 = S_3 \cos 19,5 = 283 \text{ W}$


finalement $P_T = P_1 + P_2 + P_3 = 588 \text{ W}$

$Q_T = Q_1 + Q_2 + Q_3 = 216 - 135 + 100 = 181 \text{ vars inductifs}$

$\vec{S}_T = P_T + jQ_T = 588 + j181 = 616 \angle 17,1^\circ \text{ VA}$

$S_T = 616 \text{ VA}$

$FP = \frac{P_T}{S_T} = 0,958$ inductif

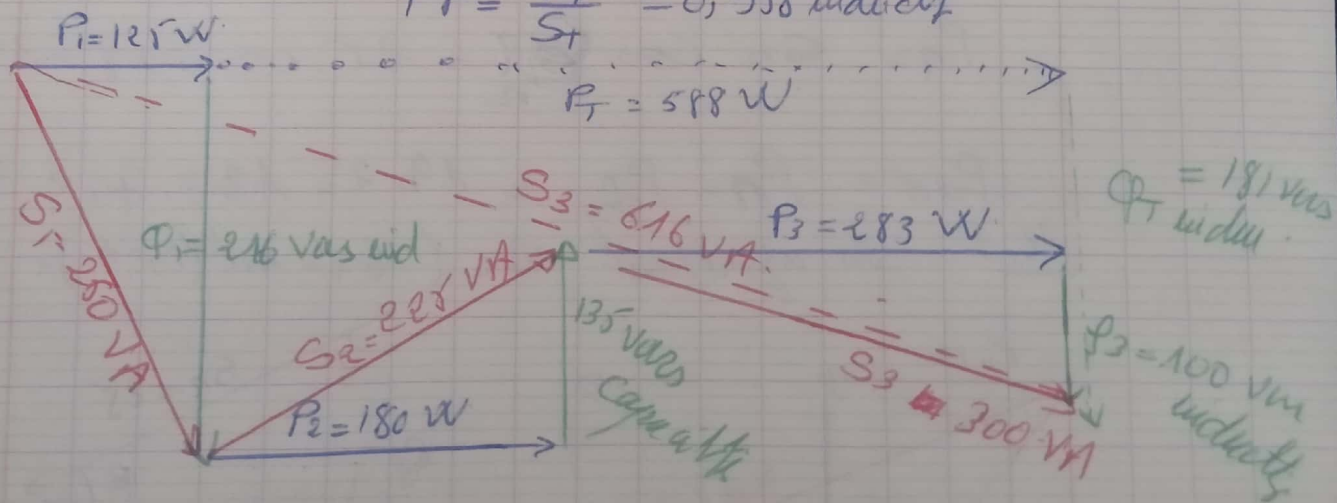


Exercice 10

$S_n = 25 \text{ KVA}$ $P_{ch} = 12 \text{ kW}$ $F_p = 0,6$ (inductif)

10/ Le taux de charge du transformateur

$P_{ch} = S_{ch} \times F_p \Rightarrow S_{charge} = \frac{P_{ch}}{F_p} = \frac{12}{0,6} = 20 \text{ KVA}$

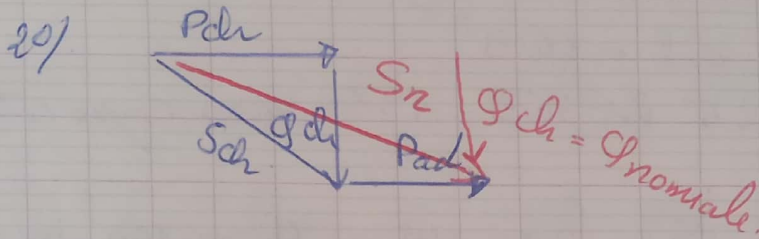$S_n \rightarrow 100\%$
 $S_{ch} \rightarrow \tau_{ch}$ } $\tau_{ch} = \frac{20 \cdot 100}{25} = 80\%$



La charge additionnelle possède un $F_{pad} = 1$

$\Rightarrow Q_{pad} = 0 \text{ var}$

$\Rightarrow Q_{ch} = \text{reste inchangeable}$

$Q_{ch} = Q_n = S_n \sin 53,1 = 16 \text{ Kvars inductif}$


$F_{pn} = ?$ $Q_n = S_n \sin \epsilon_n \Rightarrow \epsilon_n = \arcsin\left(\frac{16}{25}\right)$

$\epsilon_n = 39,8^\circ$

$P_n = S_n \cos \epsilon_n = 25 \cdot \cos 39,8 = 19,2 \text{ kW}$

$P_{ad} = P_n - P_{ch} = 19,2 - 12 = 7,2 \text{ kW}$

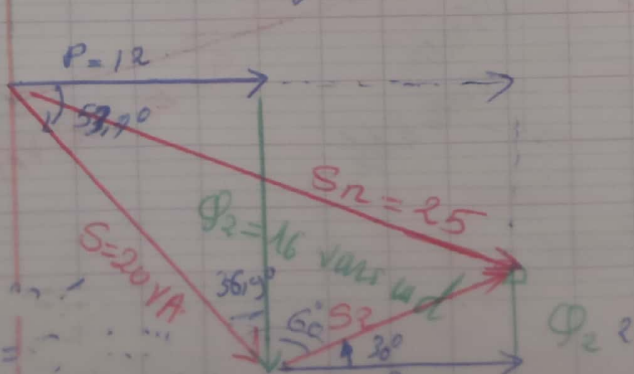10.3 en ajoutant S_2 ($\epsilon_2 = \arcsin(0,86) = 30^\circ$)



Suite à l'exo 10.

$$P_2 = S_2 \cos 30 = \frac{\sqrt{3}}{2} S_2$$

$$Q_2 = S_2 \sin 30 = \frac{1}{2} S_2$$

$$S_n^2 = (P_{ch} + P_2)^2 + (Q_{ch} - Q_2)^2$$

$$25^2 = \left(12 + \frac{\sqrt{3}}{2} S_2\right)^2 + \left(16 - \frac{1}{2} S_2\right)^2$$

$$25^2 = 12^2 + 16^2 + (12\sqrt{3} - 16)S_2 + \left(\frac{3}{4} + \frac{1}{4}\right)S_2^2$$

La résolution de cette eq du second

Ordre donne $\Rightarrow S_2 = 12,8 \text{ kVA}$

$$P_2 = 12,8 \cdot \frac{\sqrt{3}}{2} = 11,1 \text{ kW}$$

$$Q_2 = 6,4 \text{ vars capacitif}$$