

Exo3:

1- Courant de démarrage:

$$U = E + R_a I_a$$

Au démarrage $N=0 \Rightarrow E=0$.

$$U = R_a I_d \Rightarrow I_d = \frac{U}{R_a} = \frac{375}{4} = 93,75 \text{ A}.$$

$$I_{\max} = 2,5 \cdot I_d = 2,5 \times 3 \times 7,5 \text{ A}.$$

2- Résistance Totale:

$$I_{\max} = 7,5 \text{ A}.$$

$$U = (R_a + R_d) I_{\max} \Rightarrow R_d = \frac{U - R_a I_{\max}}{I_{\max}} = 46 \Omega.$$

3- $C_d = 1,5 \text{ en}.$

$$I_{\min} = 1,5 I_d = 4,5 \text{ A}.$$

$$E = \frac{P}{a} n N \phi = K N.$$

$$K = \frac{P}{a} n \phi = 24 \text{ UI (flux Constant)}$$



$$U = (R_a + R_d) I_{\min} + E_1$$

$$E_1 = K N_1 \Rightarrow N_1 = \frac{U - (R_a + R_d) I_{\min}}{K}$$

$$N_1 = 6,25 \text{ tr/s} = 375 \text{ tr/min}.$$

$$\left. \begin{aligned} I_{\max} (R_a + R_d) &= U \rightarrow R_d = 46 \Omega \\ I_{\min} (R_a + R_d) + K N_1 &= U \Rightarrow N_1 = 6,25 \text{ tr/s} \end{aligned} \right\}$$
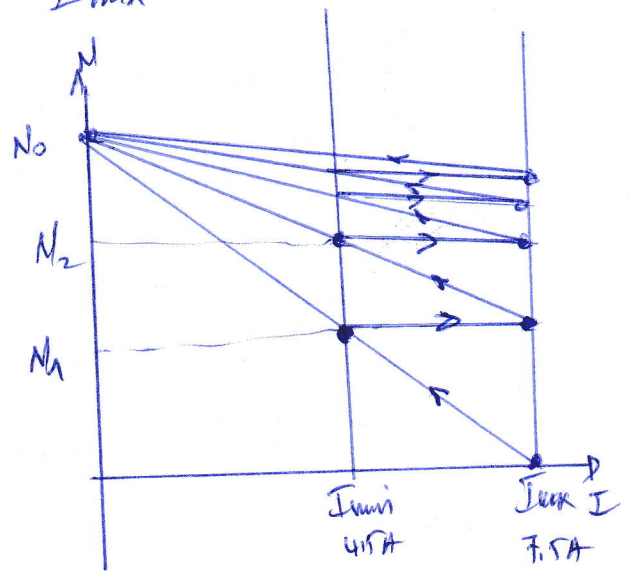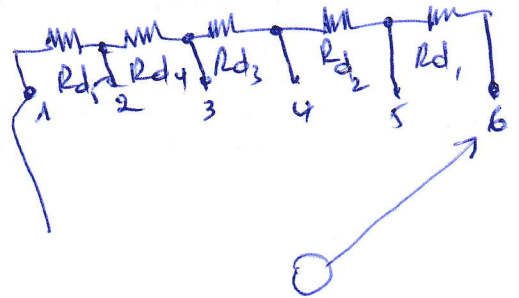
$$\left. \begin{aligned} I_{\max} (R_a + R_d - R_2) + K N_1 &= U \Rightarrow R_{d1} = 20 \Omega \\ I_{\min} (R_a + R_d - R_4) + K N_2 &= U \Rightarrow N_2 = 10 \text{ tr/min} \end{aligned} \right\}$$



6 plots $\rightarrow$ 20 resistance

Exo3:

1- Courant de démarrage:

$$U = E + R_a I_a$$

Au démarrage $N=0 \Rightarrow E=0$.

$$U = R_a I_d \Rightarrow I_d = \frac{U}{R_a} = \frac{375}{4} = 93,75 \text{ A.}$$

$$I_{\max} = 2,5 \cdot I_d = 2,5 \times 3 \times 7,5 \text{ A.}$$

2- Résistance Totale:

$$I_{\max} = 7,5 \text{ A.}$$

$$U = (R_a + R_d) I_{\max} \Rightarrow R_d = \frac{U - R_a I_{\max}}{I_{\max}} = 46 \Omega.$$

3- $C_d = 1,5 \text{ en.}$

$$I_{\min} = 1,5 I_d = 4,5 \text{ A.}$$

$$E = \frac{P}{a} n N \phi = k N.$$

$$k = \frac{P}{a} n \phi = 24 \text{ UI (flux Constant)}$$



$$U = (R_a + R_d) I_{\min} + E_1$$

$$E_1 = k N_1 \Rightarrow N_1 = \frac{U - (R_a + R_d) I_{\min}}{k}$$

$$N_1 = 6,25 \text{ tr/s} = 375 \text{ tr/min.}$$

$$\left. \begin{aligned} I_{\max} (R_a + R_d) &= U \rightarrow R_d = 46 \Omega \\ I_{\min} (R_a + R_d) + k N_1 &= U \Rightarrow N_1 = 6,25 \text{ tr/s.} \end{aligned} \right\}$$
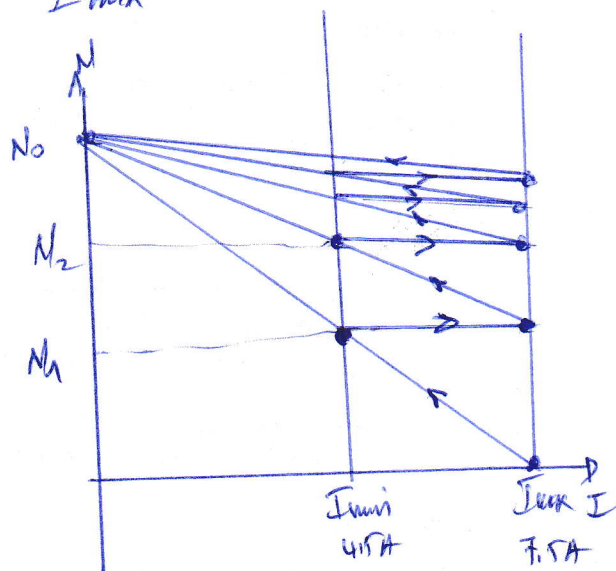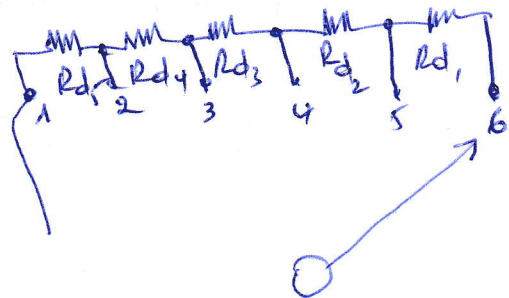
$$\left. \begin{aligned} I_{\max} (R_a + R_d - R_2) + k N_1 &= U \Rightarrow R_{d1} = 20 \Omega \\ I_{\min} (R_a + R_d - R_4) + k N_2 &= U \Rightarrow N_2 = 10 \text{ tr/min} \end{aligned} \right\}$$



6 plots $\rightarrow$ 20 resistance

$$\begin{cases}
 F_{\max}(R_a + R_d - R_{d1} - R_{d2}) + kN_2 = U \Rightarrow R_{d2} = 12 \Omega \\
 F_{\min}(R_a + R_d - R_{d1} - R_{d2}) + kN_3 = U \Rightarrow N_3 = 12,25 \text{ Tr/s} \\
 F_{\max}(R_a + R_d - R_{d1} - R_{d2} - R_{d3}) + kN_3 = U \Rightarrow R_{d3} = 7,2 \Omega \\
 F_{\min}(\quad \quad \quad) + kN_4 = U \Rightarrow N_4 = 13,65 \text{ Tr/s} \\
 \quad \quad \quad \Rightarrow R_{d4} = 4,48 \Omega \\
 \quad \quad \quad \Rightarrow N_5 = 14,44 .
 \end{cases}$$

$$R_{d5} = R_d - \sum_{i=1}^4 R_{di} = 2,32 \Omega .$$